

Exercises to the lecture
Complexity Theory
Sheet 10

Prof. Dr. Roland Meyer

M.Sc. Peter Chini

Delivery until 20.01.2016 at 12h

Exercise 10.1 (Unbounded Fan-In)

Let g be a gate in a circuit. The **Fan-In** of g is the in-degree of g , the number of incoming edges. A circuit has Fan-In **bounded by** $k \in \mathbb{N}$ if for any gate in the circuit, the Fan-In is bounded by k . In the lecture we considered circuits with Fan-In bounded by 2. This exercise shows that we can always restrict to this case:

Let C be a circuit with n input variables and unbounded Fan-In. Moreover, let $size(C) = s$ and $depth(C) = d$. Show that there is a circuit C' that has Fan-In bounded by 2 and

- $C'(x) = C(x)$ for all inputs x ,
- $size(C') \in \mathcal{O}(s^2)$ and
- $depth(C') \in \mathcal{O}(d \cdot \log s)$.

In particular, if $s(n)$ is a polynomial and $d(n)$ is a constant, we get: $depth(C') \in \mathcal{O}(\log n)$.
Hint: Gates of Fan-In greater than 2 must be replaced. How can you do this? You also need a bound for the maximal Fan-In of a gate in C .

Exercise 10.2 (Addition with parallel carry computation)

In this exercise we want to solve the **addition problem** using circuits:

Input: $2n$ variables a_1, \dots, a_n and b_1, \dots, b_n , the binary representation of two natural numbers a and b .

Output: $n + 1$ variables s_1, \dots, s_{n+1} , the binary representation of $s = a + b$.

A first approach to this problem would use *full adders*. A full adder for the i -th bits would compute $a_i + b_i + c_i$, where c_i is the carry, and it would output the sum bit and a new carry bit. This new carry bit could then be used as input for the full adder for the $(i + 1)$ -st bits. This circuit would have depth $\mathcal{O}(n)$. We want to do better:

- a) Construct a circuit \mathcal{G}_i with unbounded Fan-In that computes the i -th carry bit c_i and has size $\mathcal{O}(i)$ and constant depth.

Hint: In contrast to the circuit described above, the computation of c_i should not depend on c_{i-1} . Note that c_i is 1 if and only if there is a position $j < i$, where the carry is generated and propagated to position i . Construct a Boolean formula for this condition - this may also depend on a_1, \dots, a_{i-1} and b_1, \dots, b_{i-1} . Then transform the formula into a circuit.

- b) Use Part a) to construct a circuit for the addition problem that has size $\mathcal{O}(n^2)$ and constant depth.
- c) Conclude that there is a circuit of Fan-In bounded by 2 that solves the addition problem and has polynomial size and logarithmic depth.

Exercise 10.3 (Logspace reductions and the class NC)

Let A, B be two languages so that $A \leq_m^{\log} B$ and $B \in \text{NC}$. Show that in this case, also A is in NC.

Delivery until 20.01.2016 at 12h into the box next to 34-401.4